

Western New England University
College of Engineering
ECE Department
RF & Microwave Active Circuit Design
EE 456/556
Spring 2025
Design Project #1
Due: February 24, 2025

Name: Steven Placzek _____

References: Ryan Leonard _____

Aidan Butler _____

Matt Saloio _____

Design Project #1

Element	Score	Max
Design		100
Input Matching Network		100
Output Matching Network		100
Simulations (MATLAB)		200
Simulations (ADS – Ideal TRLs)		100
Comparison		100
Presentation		100
Overall		800

Western New England University

EE 456

Design Project 1

by Steven Placzek

The objective of this project was to develop an amplifier that achieves maximum gain at 15 GHz using the MGF4941AL super-low noise InGaAs HeMT biased at $V_{DS} = 2 \text{ V}$ and $I_{DS} = 10 \text{ mA}$.

NAME
Steven Placcek
SMITH CHART FORM ZY-01-N

EF 456-Design Project 1

DATE 2/22/25

DATE / /

IMN 1
2/22/25



$$\frac{7}{4} = 1,7500$$

$$\frac{2}{4} = 0,5000$$

$$d_{ca} = d_{stap} - d_{stent}$$

$$d_{b2} = 0,137$$

$$\theta_{a2} = 40,320^\circ$$
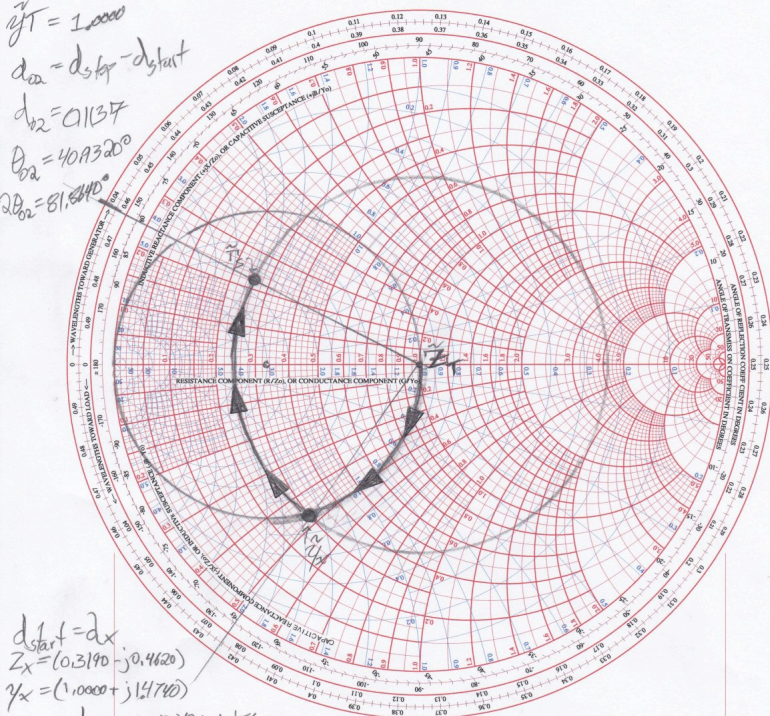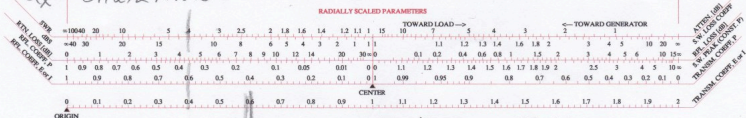
$$2\theta_{a2} = 81,640^\circ$$

$$d_{\text{start}} = d_x$$


$$VSWR = 0.5871$$

$$T_L = (0.5871 + 152.4480^\circ)$$

NAME
Steven Parzcek

TITLE
EE 456-Design Project 1


DWG. NO. IMN 2
DATE 2/22/25

$d_{11} = d_{stop} - d_{start}$
 $d_{11} = 0.0759\lambda$
 $\theta_{11} = 27.3240^\circ$
 $20_{11} = 54.64800$

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES


$d_{stop} = d_{stub}$
 $d_{stub} = 0.0759 \text{ WTG}$

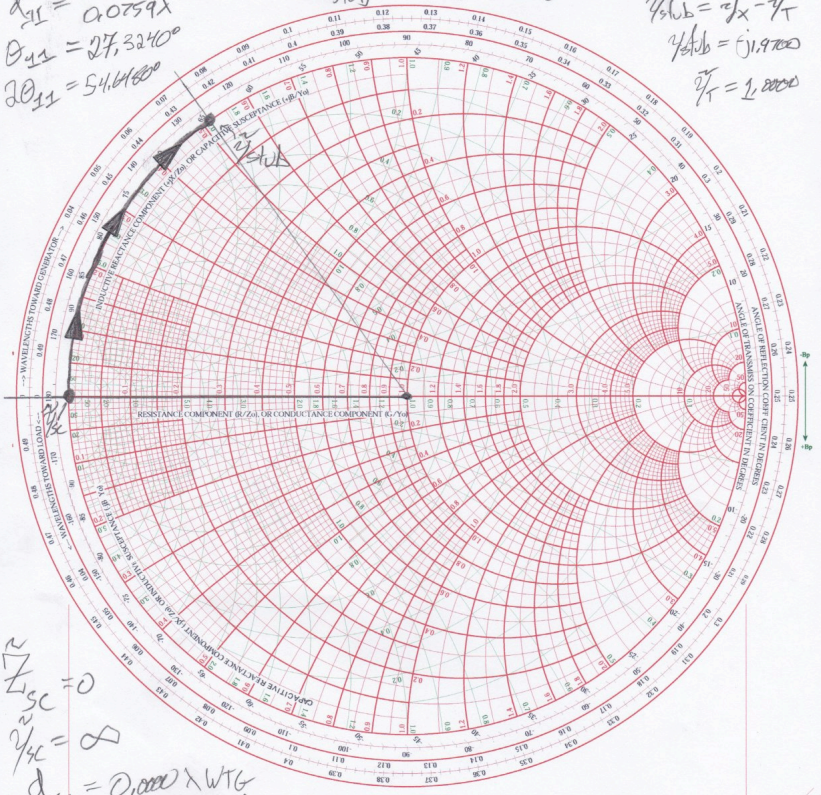$\tilde{\gamma}_x = 1.000 - j1.700$
 $\tilde{\gamma}_{stub} = \tilde{\gamma}_x - \tilde{\gamma}_T$
 $\tilde{\gamma}_{stub} = (j1.700)$
 $\tilde{\gamma}_T = 1.0000$



$Z_{sc} = 0$
 $\tilde{\gamma}_{sc} = \infty$
 $d_{sc} = 0.000 \times \text{WTG}$
 $d_{start} = d_{sc}$

RADIALLY SCALED PARAMETERS

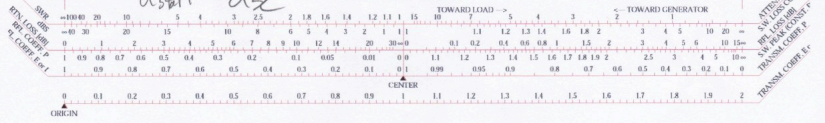

NAME Steven Placzek	TITLE EE 456 - Design Project 1	DWG. NO. OMN 2
SMITH CHART FORM ZY-01-N	COLOR BY J. COLVIN, UNIVERSITY OF FLORIDA, 1997	DATE 2/22/25

$d_{stub} = d_{start} \times \frac{1}{T} = 1.0000$

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

$d_{stub} = 0.4045 \times \text{WTG}$

$\tilde{Y}_x = (1.0000 + j)1.1474$


$\tilde{Y}_{stub} = \tilde{Y}_x - \tilde{Y}$

$\tilde{Y}_{stub} = j1.1474$

$d_{01} = 0.1545$

$\theta_{01} = 55.6200^\circ$

$2\theta_{01} = 111.2400^\circ$

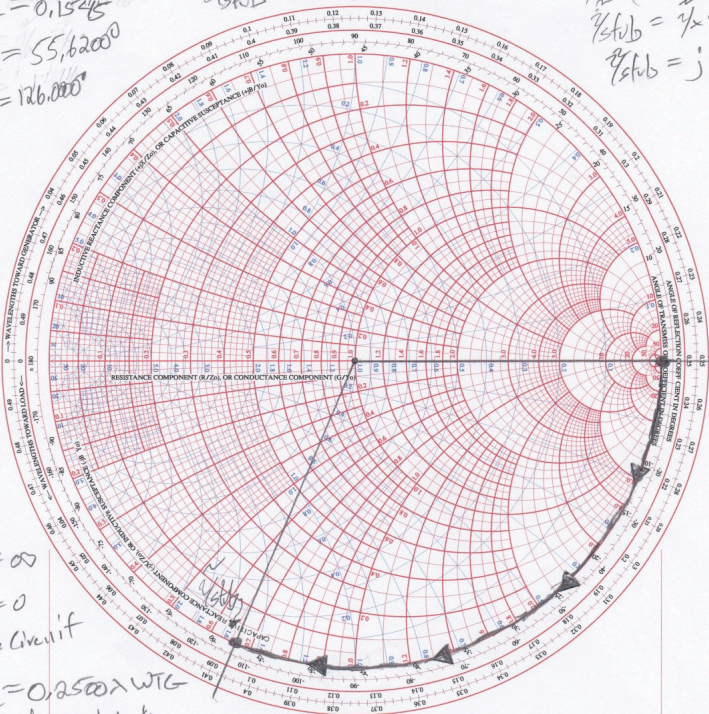

$Z_{oc} = \infty$

$Y_{oc} = 0$

Open Circuit


$d_{oc} = 0.2500 \times \text{WTG}$

$d_{oc} = d_{start}$

RADIALLY SCALED PARAMETERS

TOWARD LOAD →


← TOWARD GENERATOR

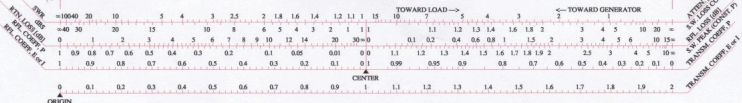

Complete Design Schematic

Amplifier Designed for Maximum Available Gain

— created using KEYSIGHT ADS SOFTWARE

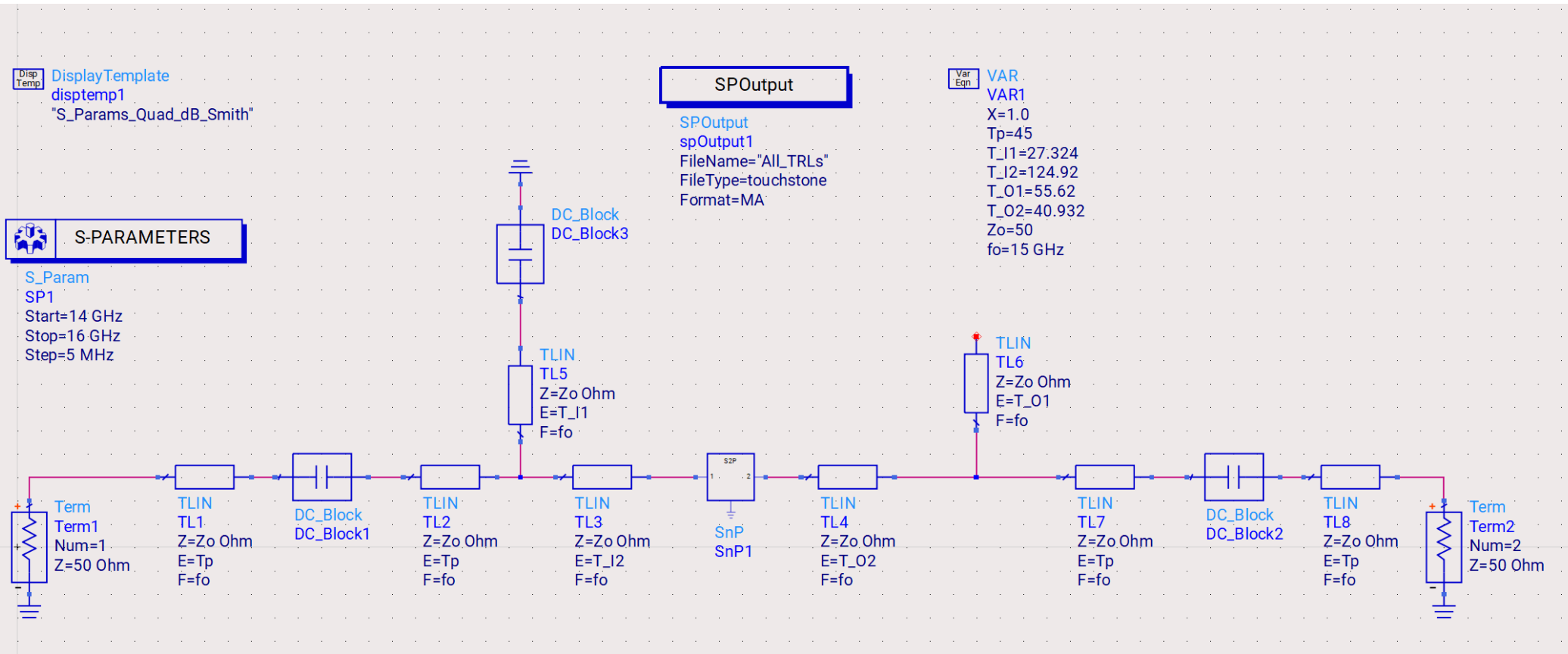

*Schematic above includes every Transmission Line and matching network within the Project Scope**

*(*All Simulations exclusively employ an Ideal Transmission Line model for Parameter Values)*

Keysight ADS Simulations


Results for the IMN

Input Matching Network


Design:

Smith Charts & S Parameters


ADS — IMN Schematic

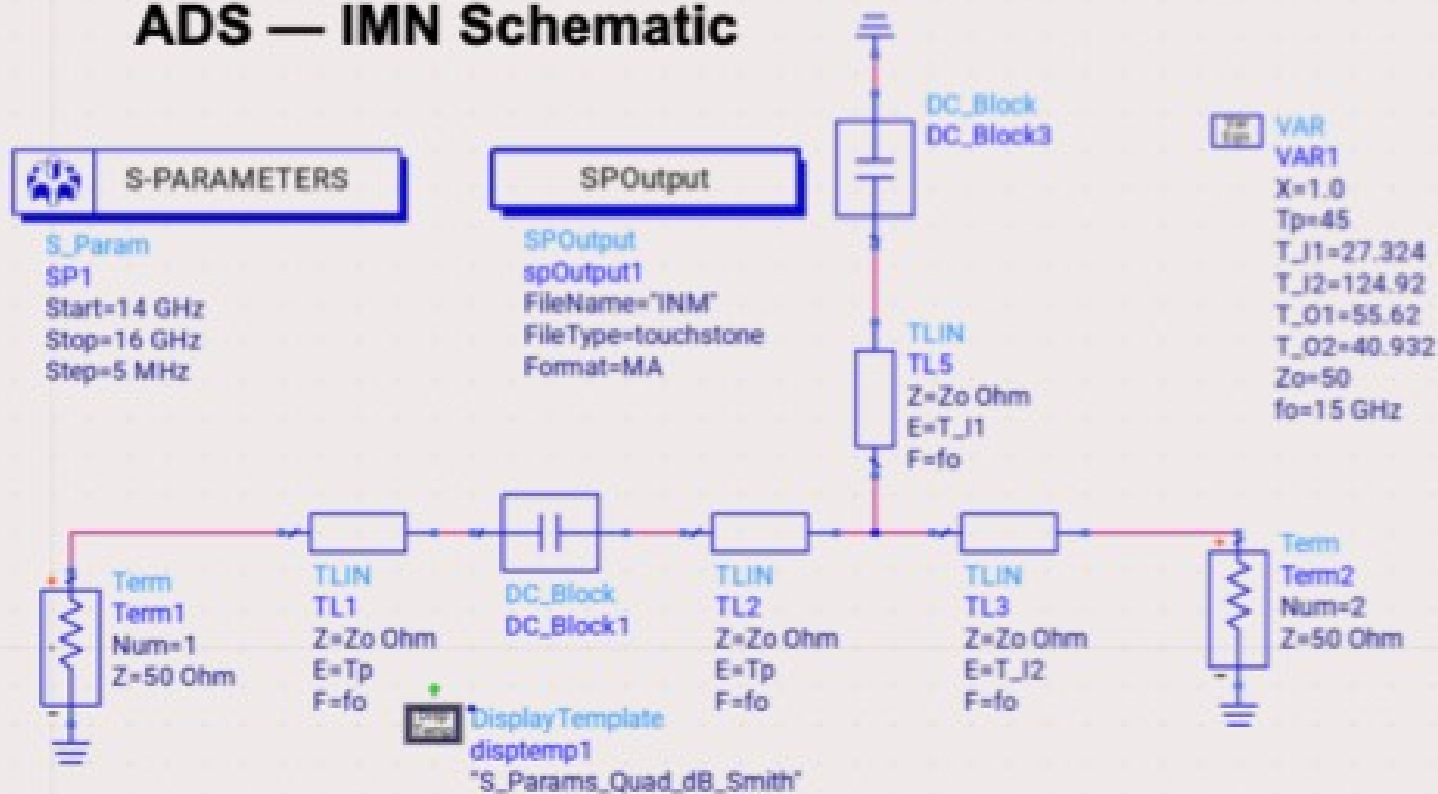

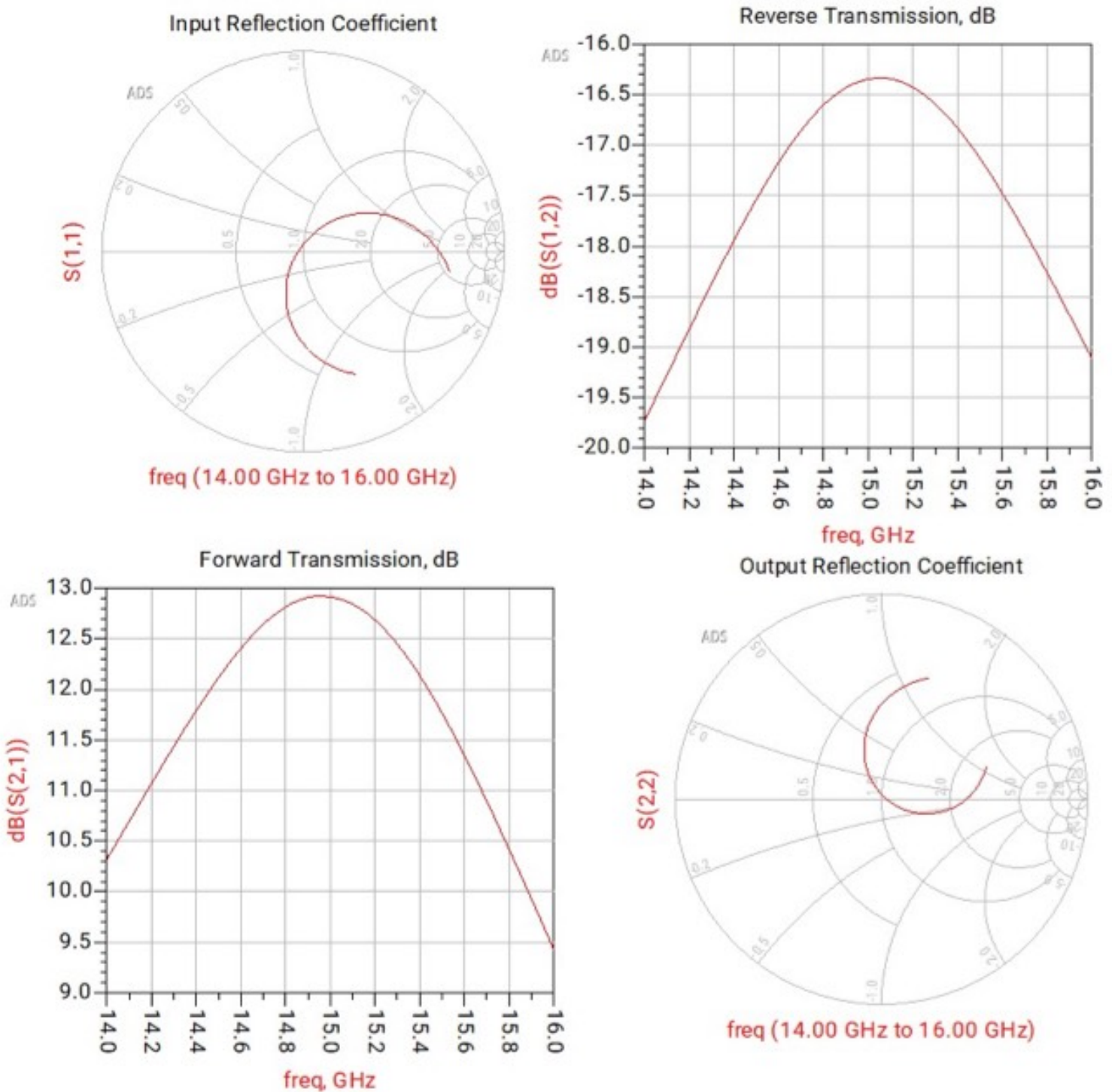
IMN Design Simulation Results: Smith Charts & S Parameters



OMN Schematic

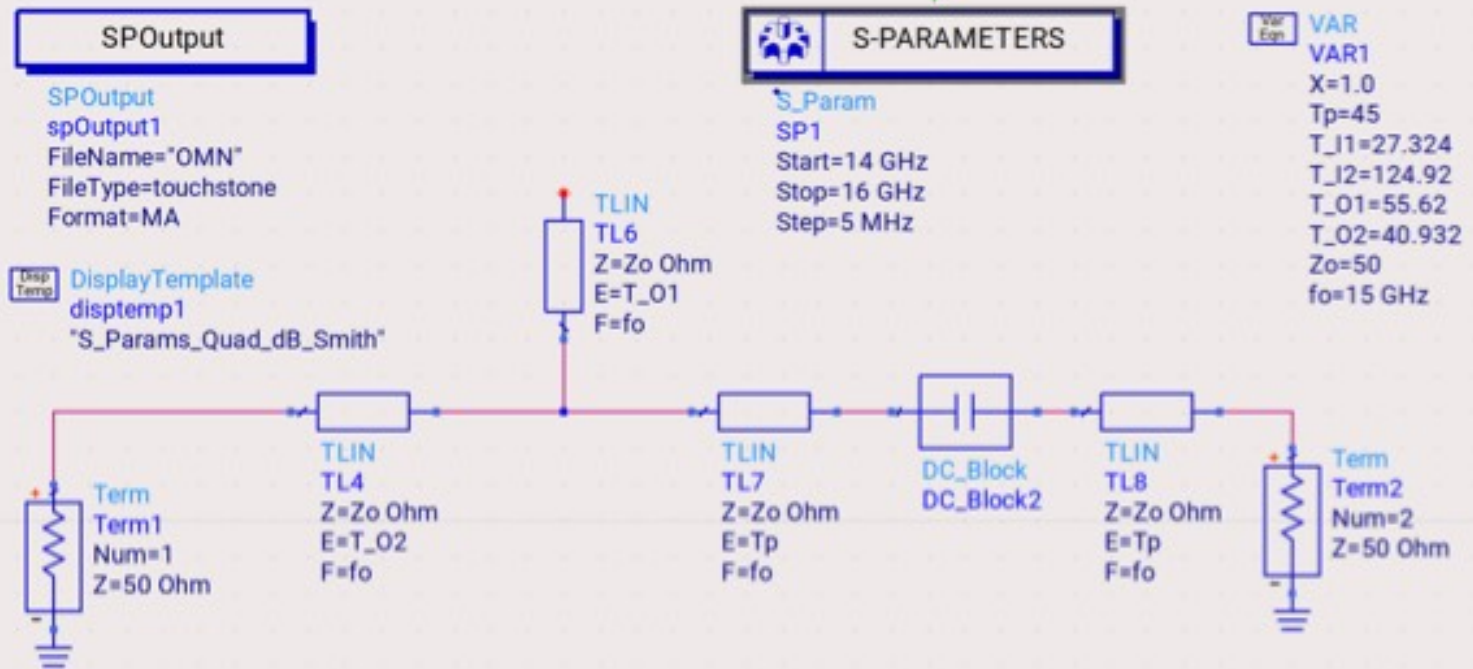


ADS – S Parameters vs Frequency Plots

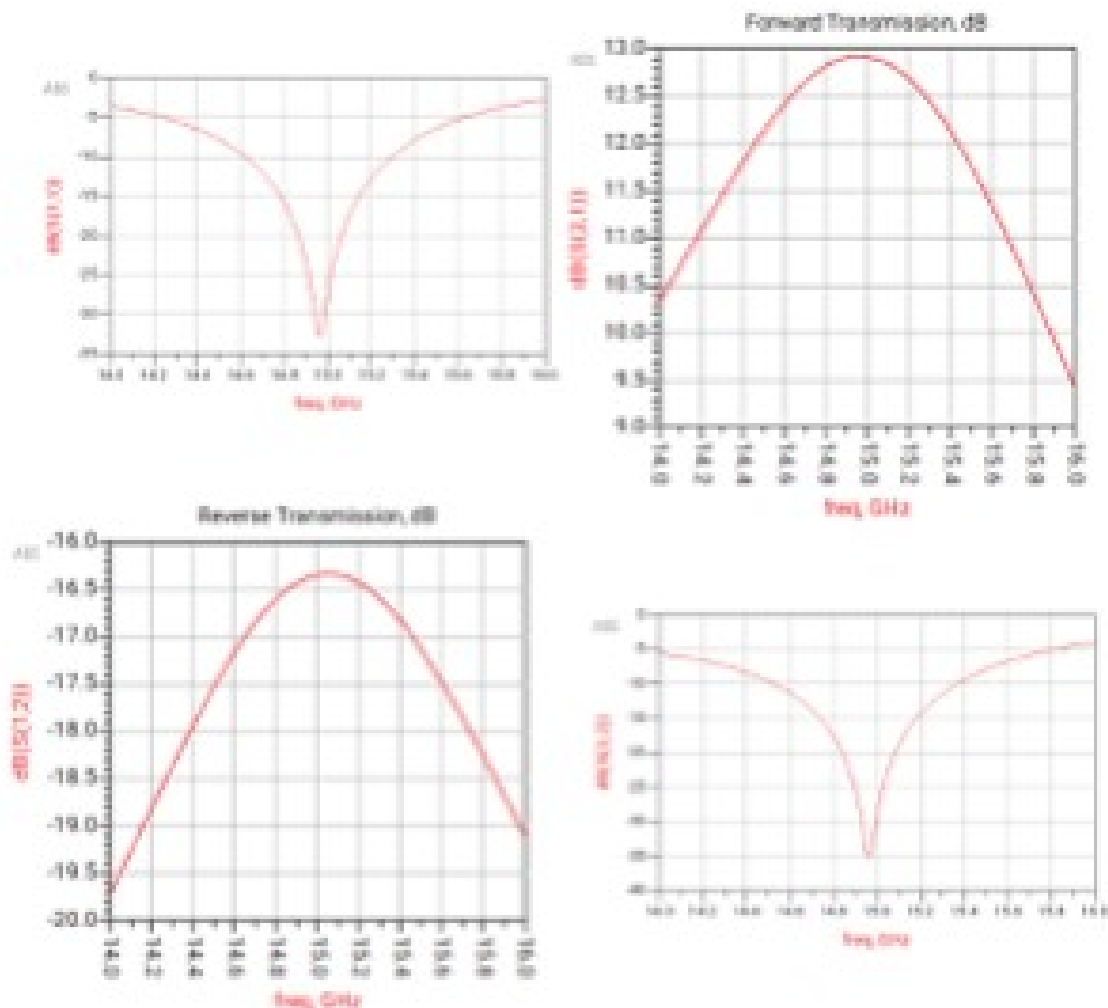

Task 4 — Part 1 — Amplifier Design Parameter Simulation via Matlab


|S₂₁| Gain (dB) vs Frequency (Hz) Plot

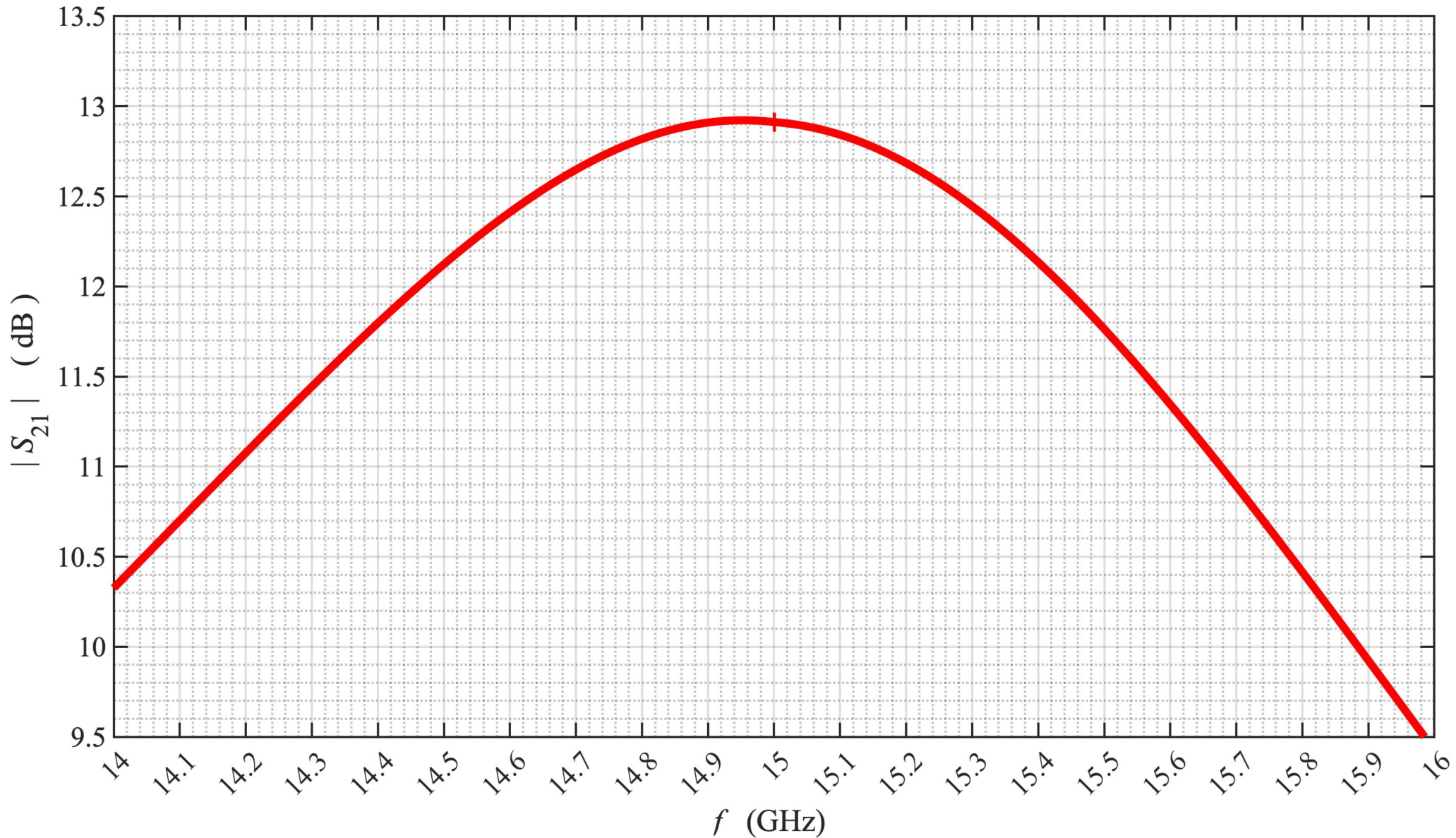

(Plot generated using Matlab)

Task 4 — Part 2 — Simulate Amplifier Design Parameters via Matlab


$|S_{11}|$ Gain (dB) vs Frequency (Hz) Plot

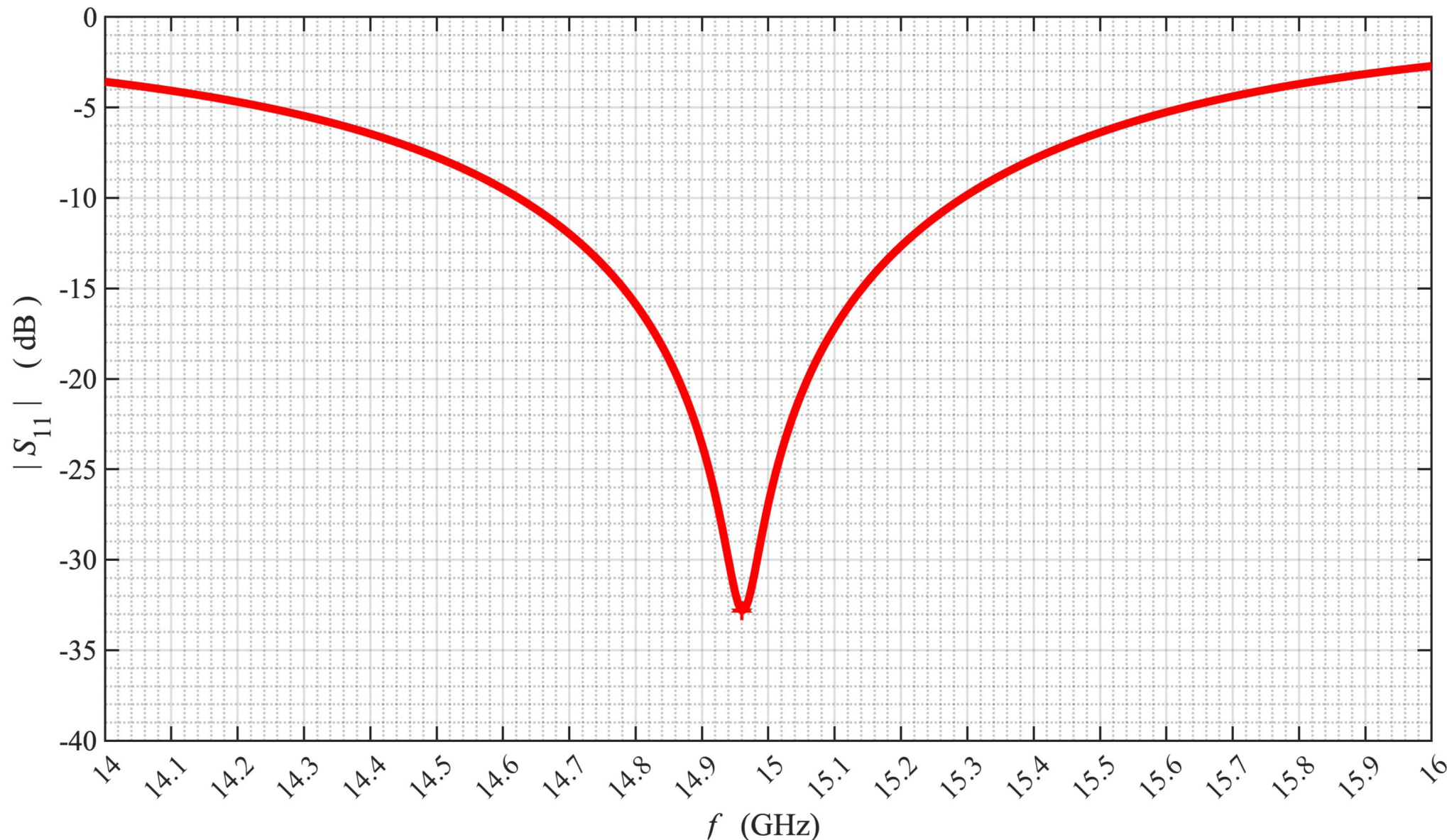

(Plot generated using Matlab)

Task 4 — Part 3 — Simulate Amplifier Design Parameters via Matlab


|S22| Gain (dB) vs Frequency (Hz) Plot

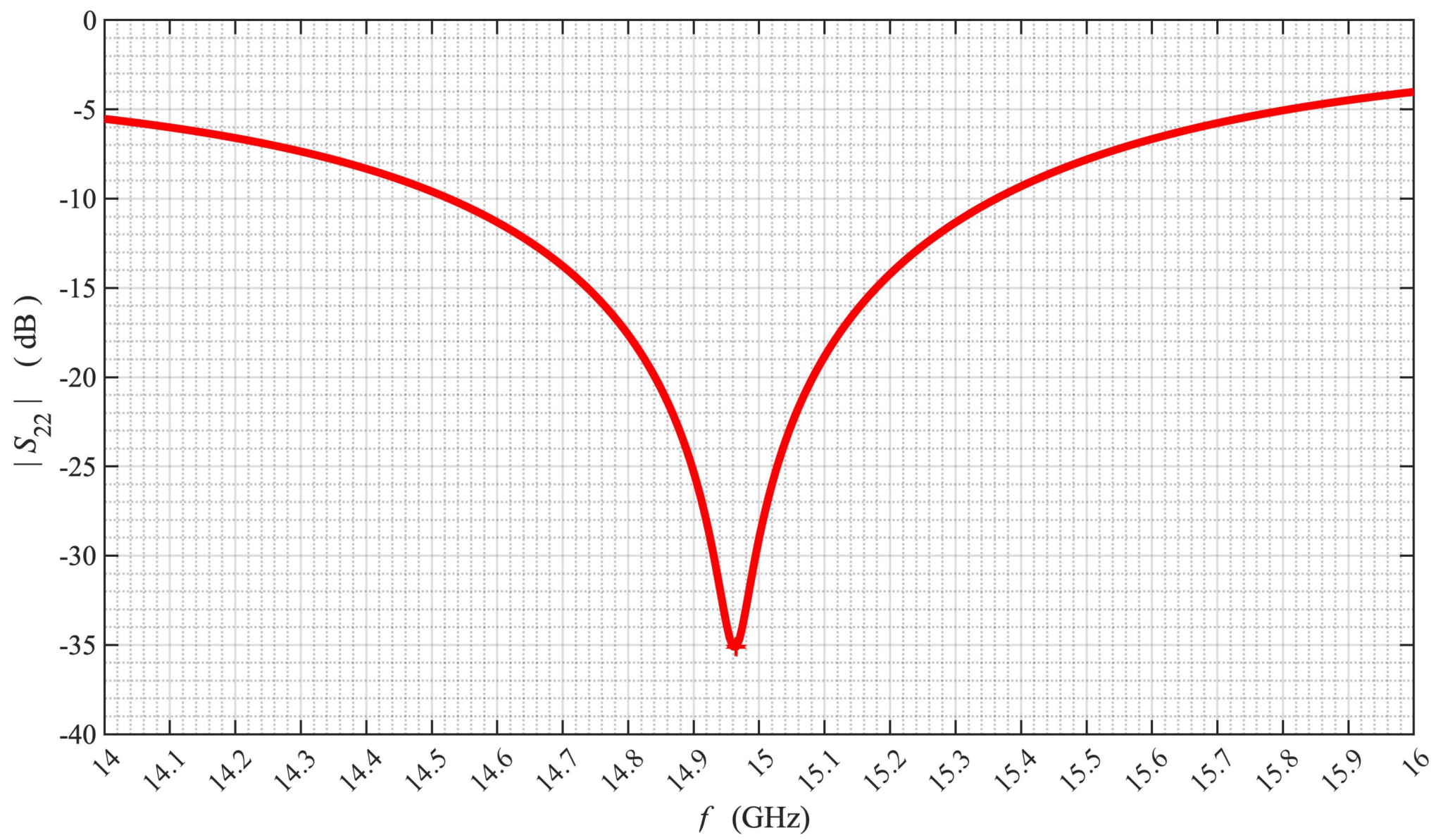

(Plot generated using Matlab)

Task 5 — Part 1 — Plotting Keysight ADS Results with Matlab

$|S_{21}|$ Gain (dB) vs Frequency (Hz) Plot

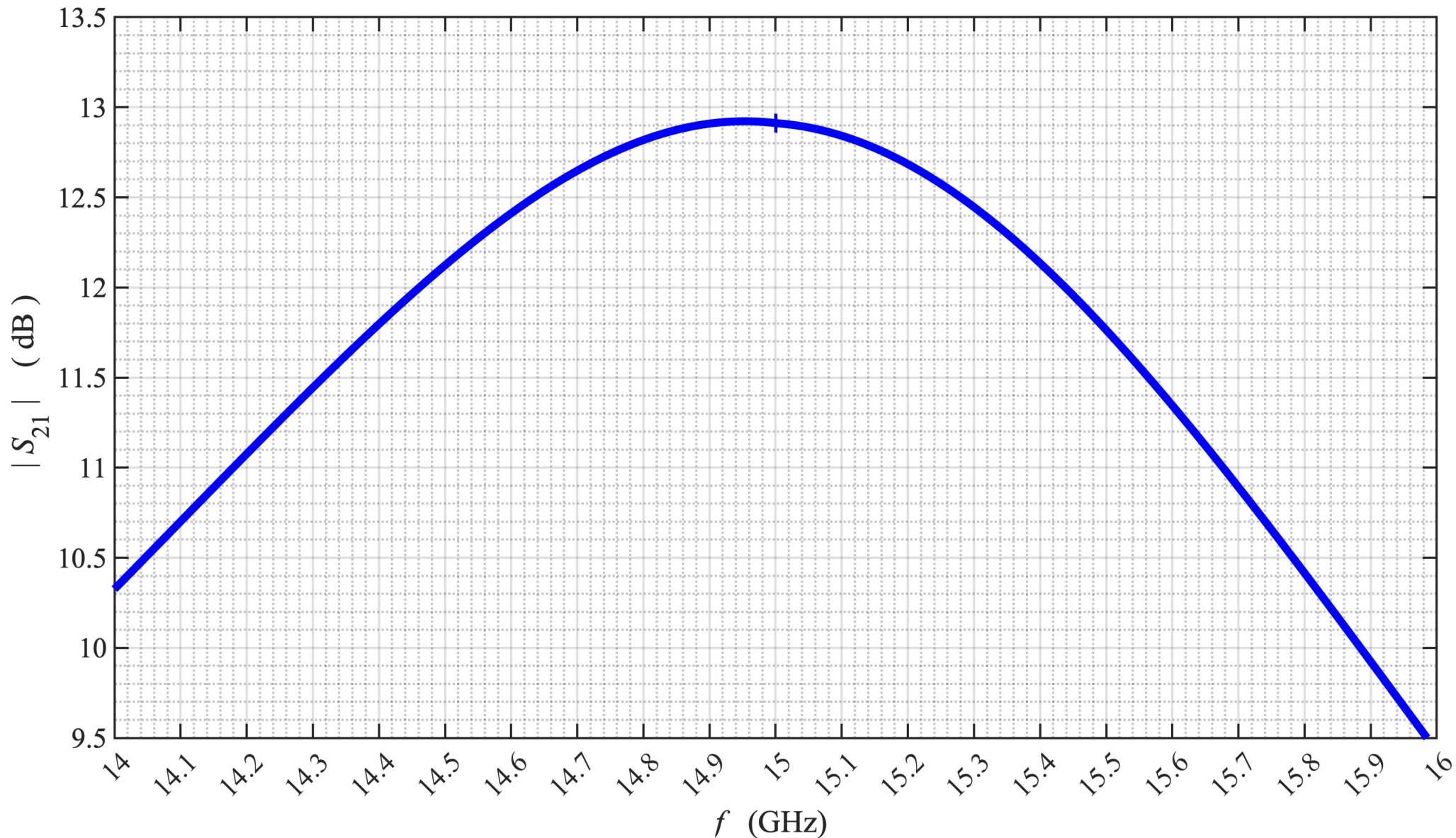


[Simulations exclusively employ Ideal Transmission Lines]

(Plot generated using Matlab)

Task 5 — Part 2 — Keysight ADS Simulation Results

$|S_{11}|$ Gain (dB) vs Frequency (Hz) Plot

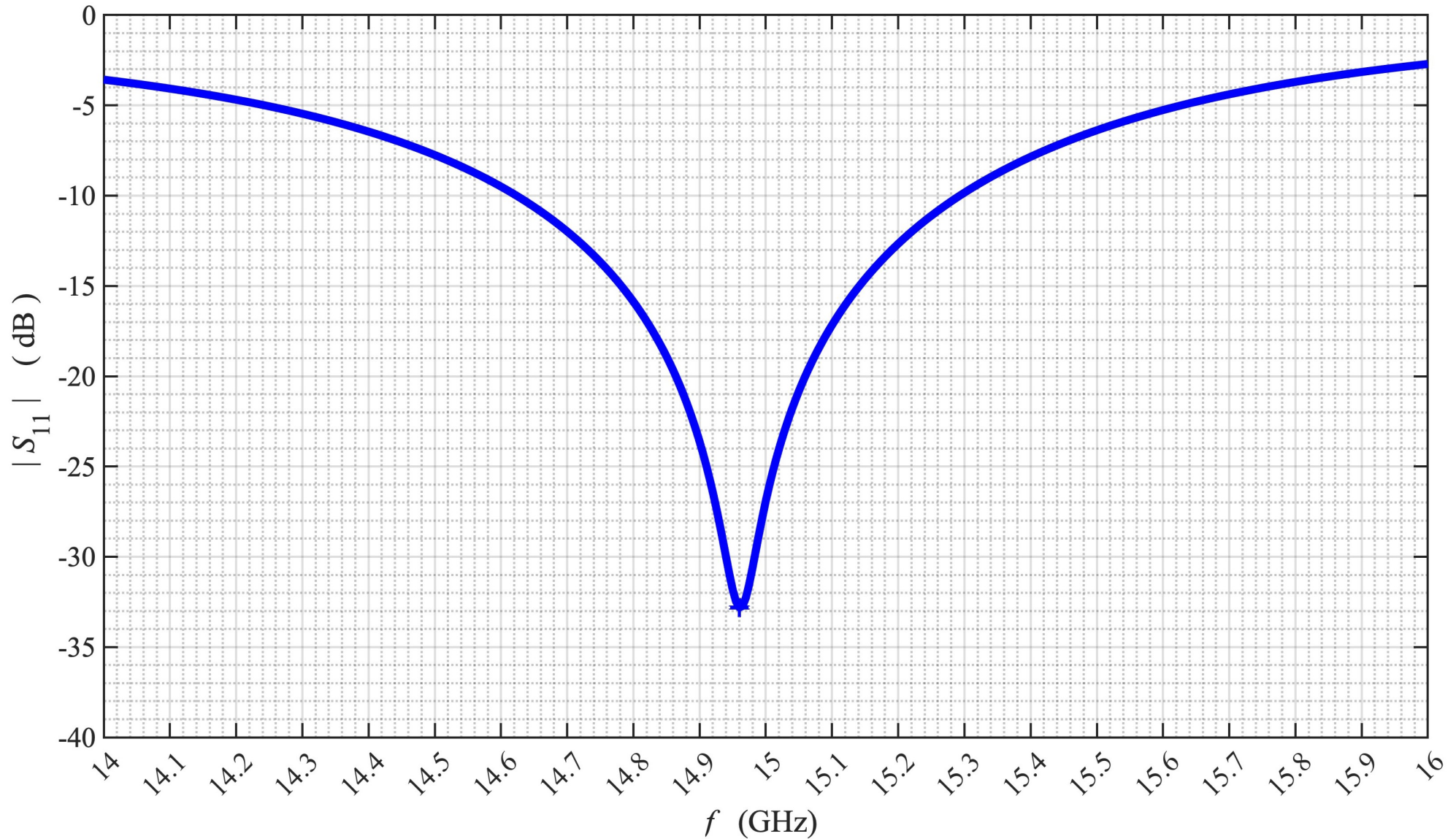


[Simulations exclusively employ Ideal Transmission Lines]

(Plot generated using Matlab)

Task 5 — Part 3 — Plotting Keysight ADS Results with Matlab

$|S_{22}|$ Gain (dB) vs Frequency (Hz) Plot

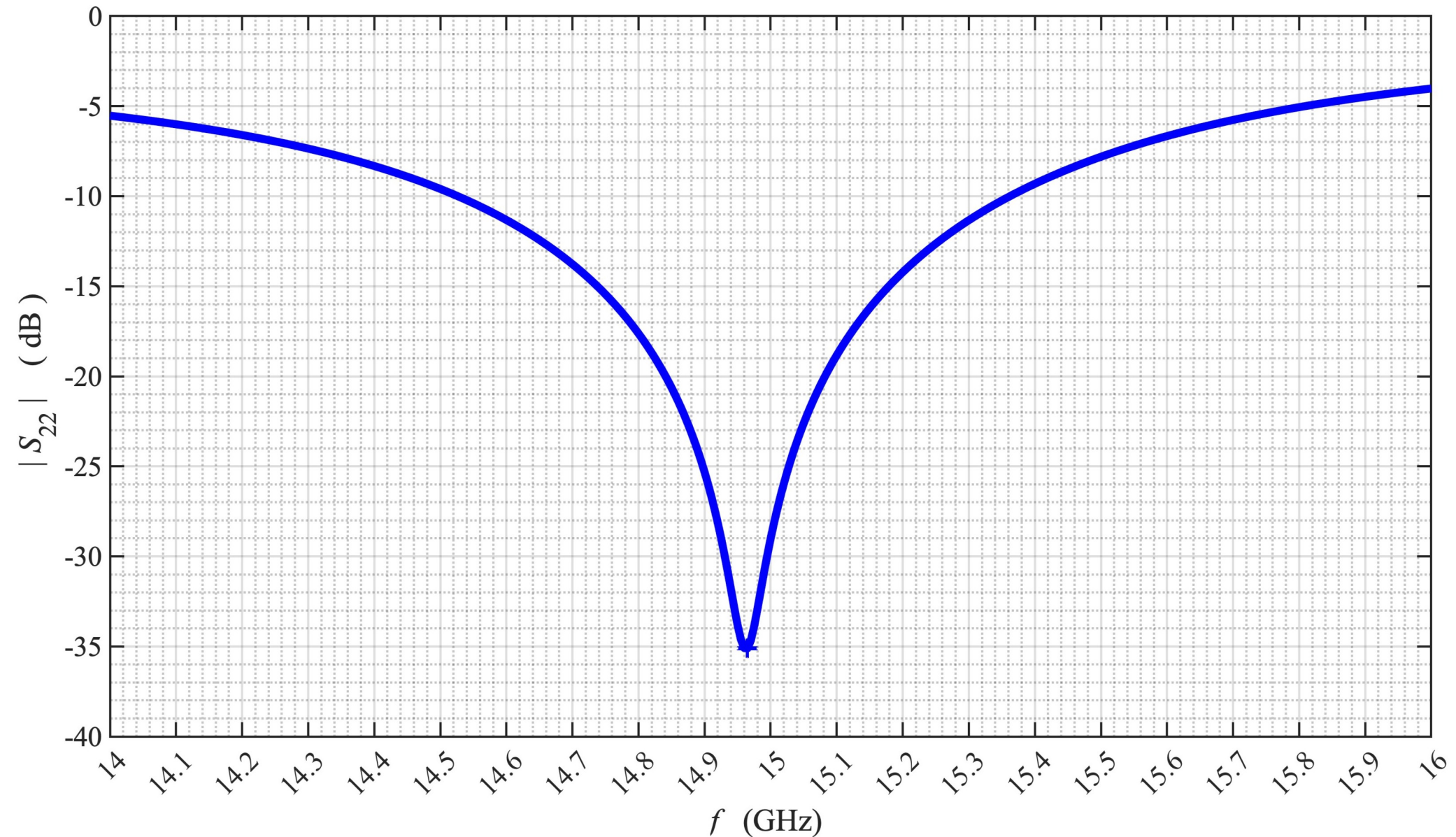


(All Simulations exclusively employ Ideal Transmission Lines)

(Plot generated using Matlab)

Task 6 — Part 2 — Matlab vs ADS Simulation Comparisons


$|S_{21}|$ Gain (dB) vs Frequency (Hz) Plot

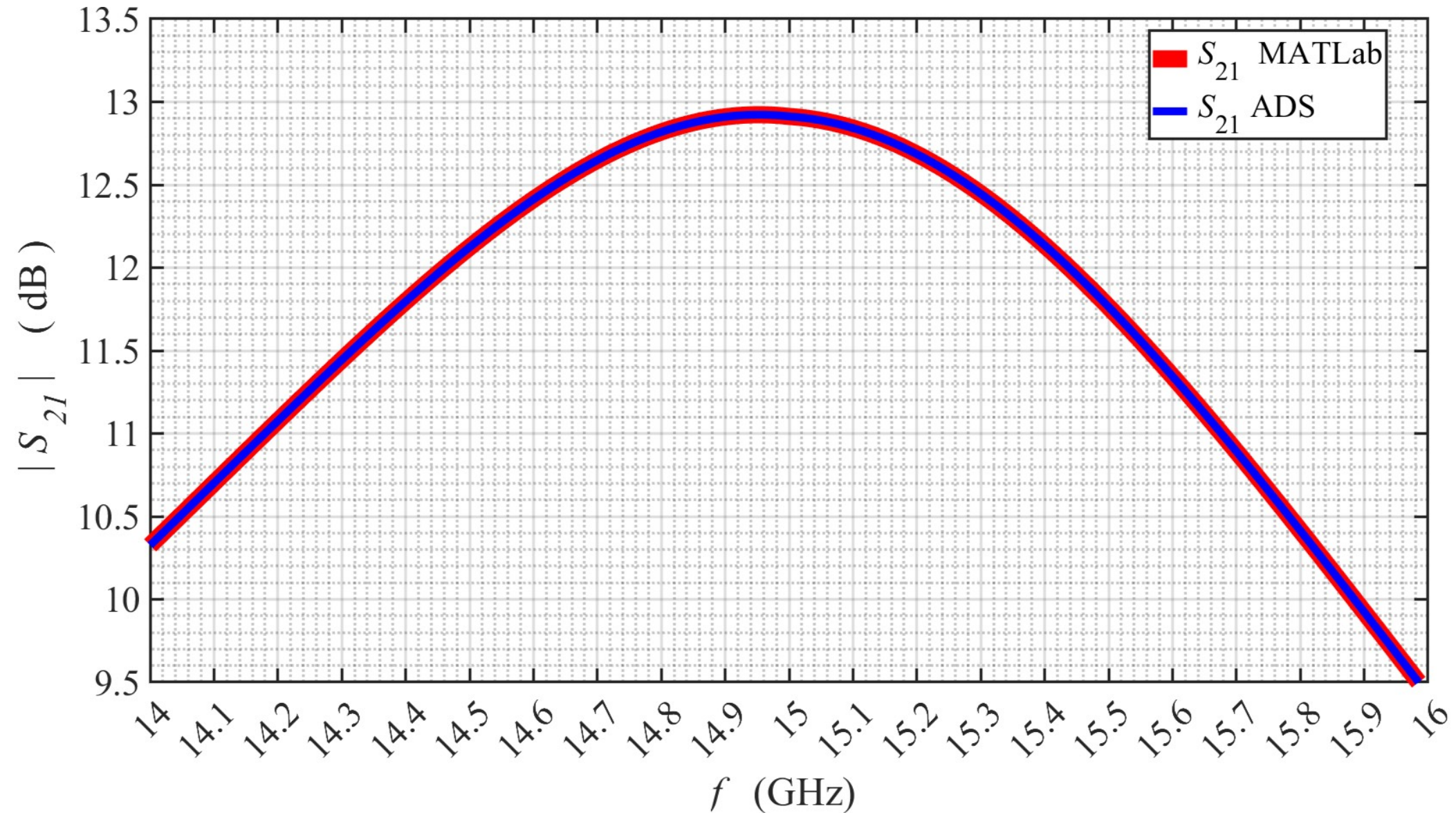

(All Simulations exclusively employ Ideal Transmission Lines)

(Plot generated using Matlab)


Task 6 — Part 2 — Matlab vs ADS Simulation Comparisons
 $|S_{11}|$ Gain (dB) vs Frequency (Hz) Plot

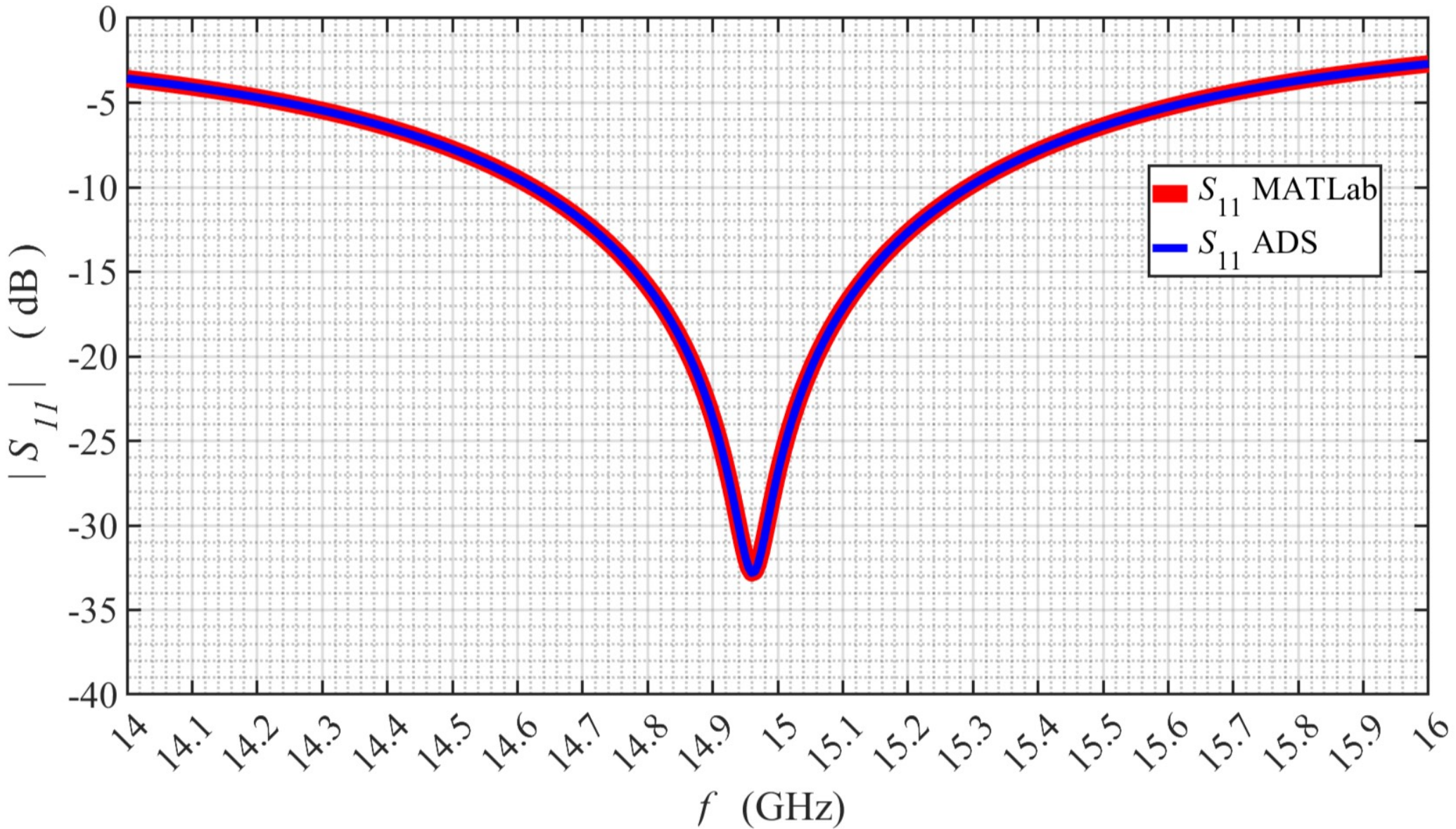

(Plot generated using Matlab)

Task 6 — Part 3 — Matlab vs ADS — Simulation Comparisons

|S₂₂| Gain (dB) vs Frequency (Hz) Plot

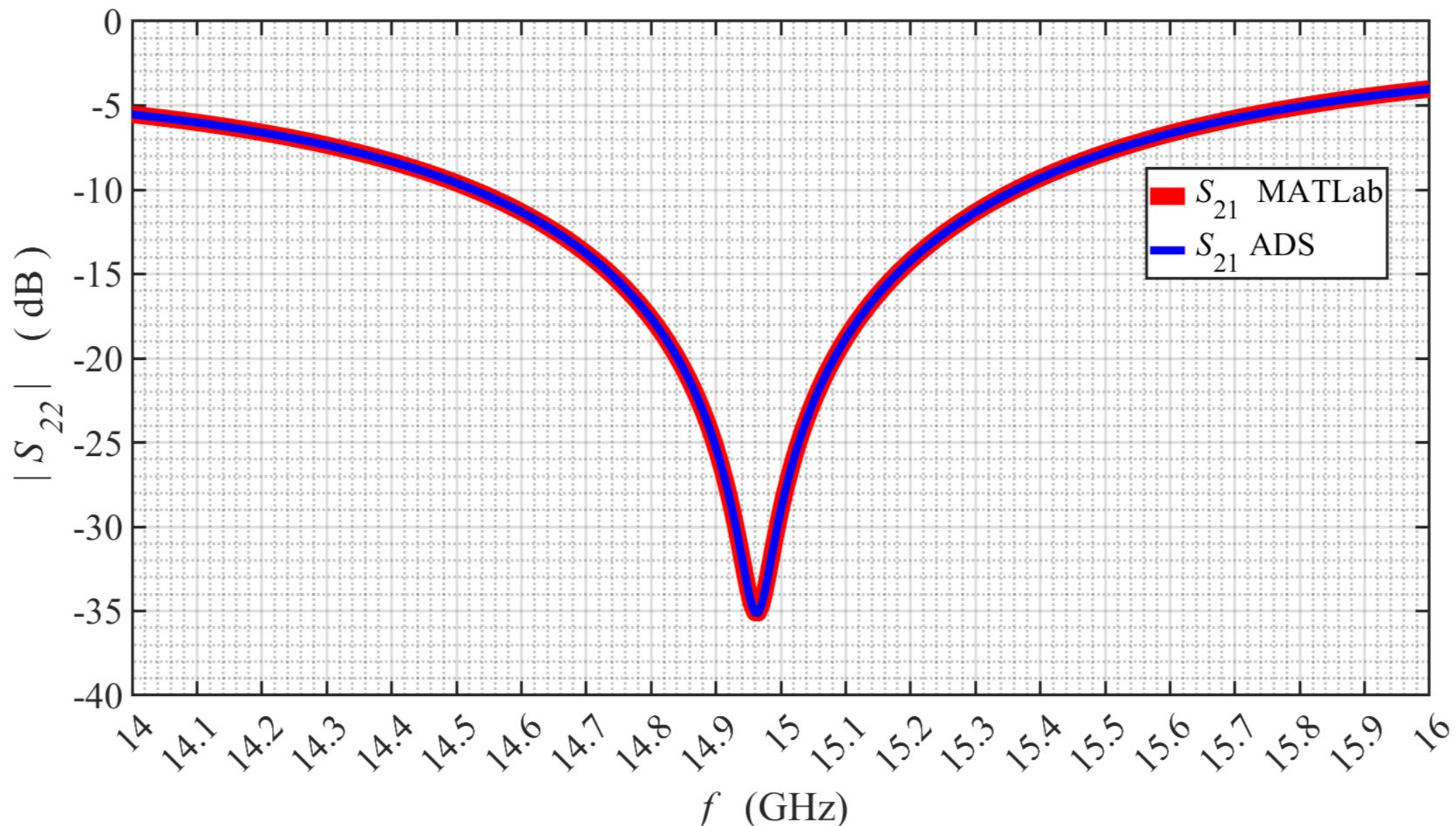

(Plot generated using Matlab)

Western New England University

EE 456

Design Project 1

Task 7: Complete Table 1

Table 1:

Parameter	Design	Simulated_MATLAB	Simulated_ADS
Γ_s	$0.7088 \angle -114.5883^\circ$	$0.6954 \angle -23.9007^\circ$	$0.6910 \angle -113.3649^\circ$
Γ_L	$0.5871 \angle 152.4980^\circ$	$0.5900 \angle 151.9775^\circ$	$0.5218 \angle 162.0738^\circ$
Γ_{in}	$0.7088 \angle 114.5883^\circ$	$0.7104 \angle 114.3690^\circ$	$0.3593 \angle 158.3169^\circ$
Γ_{out}	$0.5871 \angle -152.4980^\circ$	$0.2614 \angle -75.0200^\circ$	$0.4488 \angle -112.3242^\circ$
$ \Gamma_{IMN} $	0.0000	0.0000	0.5994
$ \Gamma_{IMN} $ (dB)	-307.0086	-0.9925	-4.4461
VSWR_IMN	1.0000	17.5223	14.8120
$ \Gamma_{OMN} $	0.0000	0.6029	0.4769
$ \Gamma_{OMN} $ (dB)	-307.4626	-4.3950	-6.4319
VSWR_OMN	1.0000	4.0366	3.7192
GT (W/W)	19.5936	19.5936	19.5527
GT (dB)	12.9211	12.9211	12.9121

EE456_Design_Project_1_Placzek_Task_7_Table_1

Parameter	Design	Simulated_MATLAB	Simulated_ADS
Γ_s	$0.7088 \angle -114.5883^\circ$	$0.6954 \angle -23.9007^\circ$	$0.6910 \angle -113.3649^\circ$
Γ_L	$0.5871 \angle 152.4980^\circ$	$0.5900 \angle 151.9775^\circ$	$0.5218 \angle 162.0738^\circ$
Γ_{in}	$0.7088 \angle 114.5883^\circ$	$0.7104 \angle 114.3690^\circ$	$0.3593 \angle 158.3169^\circ$
Γ_{out}	$0.5871 \angle -152.4980^\circ$	$0.2614 \angle -75.0200^\circ$	$0.4488 \angle -112.3242^\circ$
$ \Gamma_{IMN} $	0.0000	0.0000	0.5994
$ \Gamma_{IMN} $ (dB)	-307.0086	-0.9925	-4.4461
VSWR_IMN	1.0000	17.5223	14.8120
$ \Gamma_{OMN} $	0.0000	0.6029	0.4769
$ \Gamma_{OMN} $ (dB)	-307.4626	-4.3950	-6.4319
VSWR_OMN	1.0000	4.0366	3.7192
GT (W/W)	19.5936	19.5936	19.5527
GT (dB)	12.9211	12.9211	12.9121

Results / Analysis

- This design demonstrates excellent matching for this project, with both $VSWR_{IMN}$ and $VSWR_{OMN}$ being nearly 1. Additionally, Γ_{OMN} and Γ_{IMN} differ by less than 0.05.
- The overall gain, G_T , is very on target toward achieving the theoretical maximum, indicating an exact match.